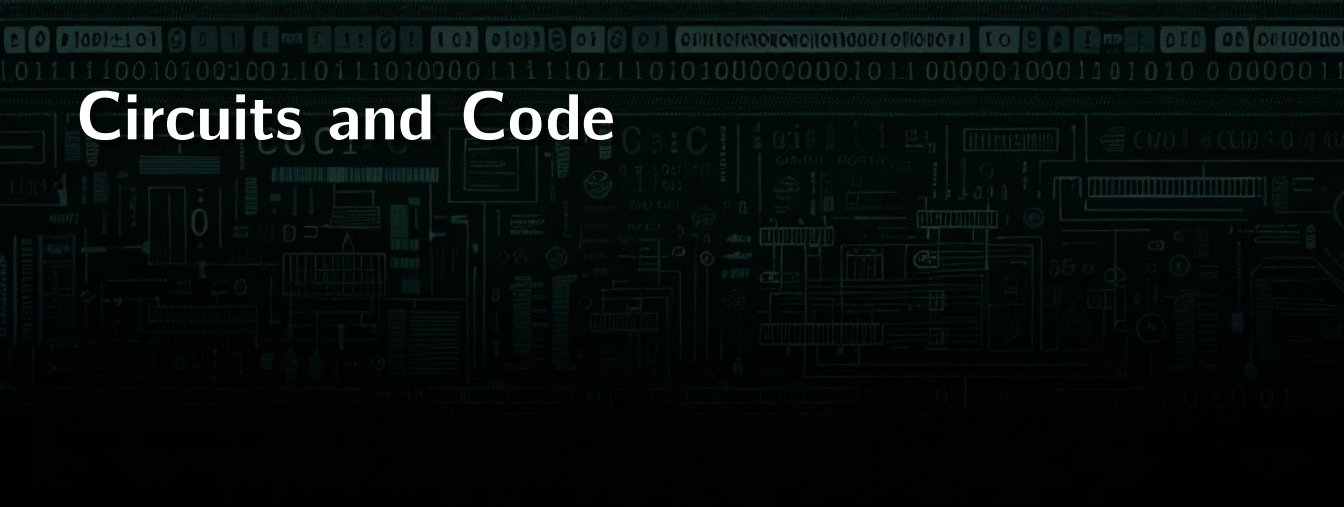





Circuits and Code

CS 2130: Computer Systems and Organization 1
September 15, 2025

Announcements


- Homework 1 due tonight
- Homework 2 available today, due next Monday

1-bit Register Circuit

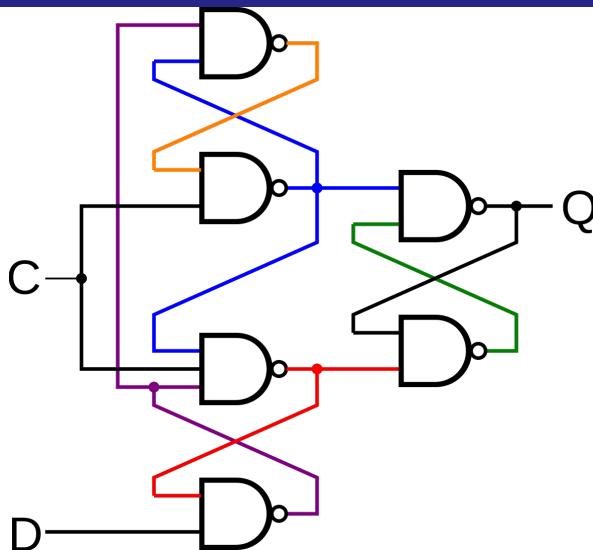


Building a Counter

Another Circuit

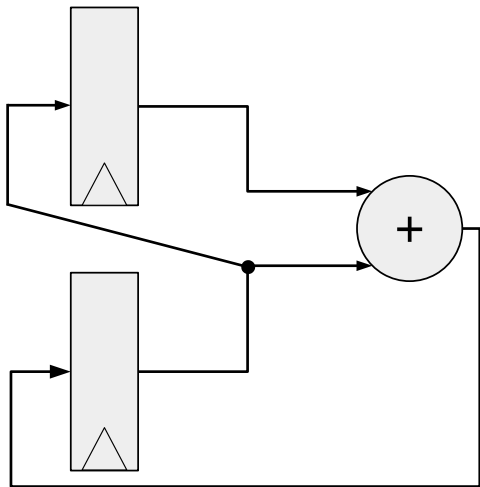

Another Circuit

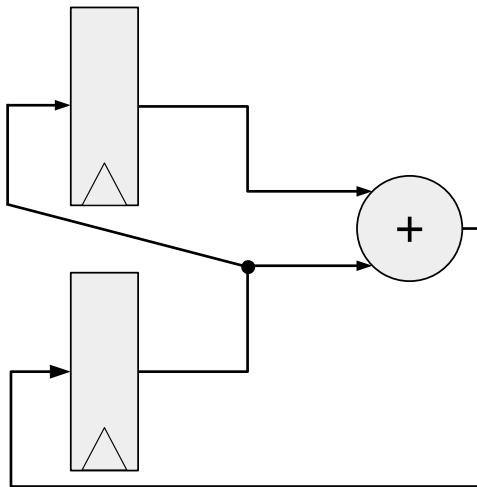

Common Model in Computers

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know: $\&$, $|$, $\wedge$, $\sim$
- Operations we can build from gates: $+$, $-$
- Others we can build:

Code to Build Circuits from Gates

Write code to build circuits from gates

- Gates we *already* know: $\&$, $|$, $\wedge$, $\sim$
- Operations we can build from gates: $+$, $-$
- Others we can build:
- Ternary operator: $?$ $:$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?
 $x = 1$
 $x = 0$

Equals

Equals: =

- Attach with a wire (i.e., connect things)
- Ex: $z = x * y$
- What about the following?
 $x = 1$
 $x = 0$
- **Single assignment:** each variable can only be assigned a value once

Subtraction

$$z = x + \sim y + 1$$

$$a = \sim y$$

$$b = a + 1$$

$$z = x + y$$

Comparisons

Each of our comparisons in code are straightforward to build:

- == - xor then nor bits of output

Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output

Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output
- `<` - consider $x < 0$

Comparisons

Each of our comparisons in code are straightforward to build:

- `==` - xor then nor bits of output
- `!=` - same as `==` without not of output
- `<` - consider `x < 0`
- `>`, `<=`, `=>` are similar


Indexing

Indexing with square brackets: []

- **Register bank** (or **register file**) - an array of registers
 - Can programmatically pick one based on index
 - I.e., can determine which register while running
- Two important operations:
 - $x = R[i]$ - Read from a register
 - $R[j] = y$ - Write to a register

Reading

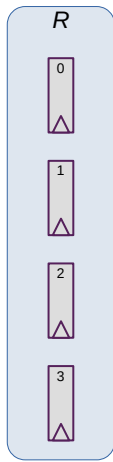$x = R[i]$ - connect output of registers to x based on index i




Aside: 4-input Mux

How do we build a 4-input mux? How many wires should i be?

Writing

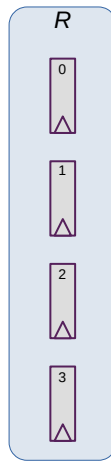$R[j] = y$ - connect y to input of registers based on index j



Aside: Creating $==0$ gates

How do we build gates that check for $j == w$?

Need one more thing to build computers

Memory and Storage

Registers

$\approx$ KiB

- 6 gates each, $\approx$ 24 transistors
- Efficient, fast
- Expensive!
- Ex: local variables

These do not persist between power cycles

Memory and Storage

Memory

≈ GiB

- Two main types: SRAM, DRAM
- DRAM: 1 transistor, 1 capacitor per bit
- DRAM is cheaper, simpler to build
- Ex: data structures, local variables

These do not persist between power cycles

Memory and Storage

Disk

≈ GiB-TiB

- Two main types: flash (solid state), magnetic disk
- Magnetic drive
 - Platter with physical arm above and below
 - Cheap to build
 - Very slow! Physically move arm while disk spins
- Ex: files

Data on disk does persist between power cycles

Putting it all together
Next time!